


Name _____ Student ID _____ Colleges & Schools _____ Department _____

Homework Unit 12

- Construct a 4-bit Johnson counter using J-K flip-flops. What sequence of states does the counter go through if it is started in state 0000? State 0110?

(Hint: refer a 3-bit Johnson counter shown below)

FIGURE 12-12
Shift Register
with Inverted
Feedback
© Cengage Learning 2014

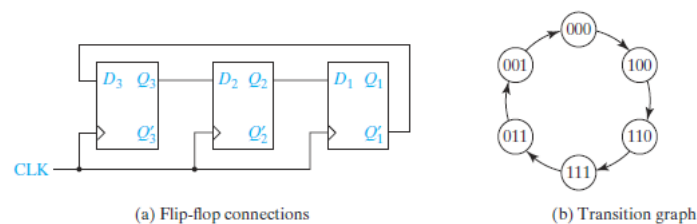

- Design a 3-bit counter using D flip-flops which counts in the sequence: 001, 100, 101, 111, 110, 010, 011, (repeat) 001, ... What will happen if the counter of is started in state 000?
- A sequential circuit contains a register of four flip-flops. Initially a binary number N ($0000 \leq N \leq 1100$) is stored in the flip-flops. After a single clock pulse is applied to the circuit, the register should contain $N + 0011$. In other words, the function of the sequential circuit is to add 3 to the contents of a 4-bit register. Design the circuit using J-K flip-flops.
- An L-M flip-flop works as follows:
 - If $LM = 00$, the next state of the flip-flop is 1.
 - If $LM = 01$, the next state of the flip-flop is the same as the present state.
 - If $LM = 10$, the next state of the flip-flop is the complement of the present state.
 - If $LM = 11$, the next state of the flip-flop is 0.
 (a) Complete the following table (use don't-cares when possible).

Present State Q	Next State Q^+	L	M
0	0		
0	1		
1	0		
1	1		

- Using this table and Karnaugh maps, derive and minimize the input equations for a counter

composed of three L-M flip-flops which counts in the following sequence: $ABC = 000, 100, 101, 111, 011, 001, (\text{repeat}) 000, \dots$