

Name _____ Student ID _____ Colleges & Schools _____ Department _____

Pretest Solutions

1. The following PLA will be used to implement the following equations:


$$X = AB'D + A'C' + BC + C'D'$$

$$Y = A'C' + AC + C'D'$$

$$Z = CD + A'C' + AB'D$$

(a) Indicate the connections that will be made to program the PLA to implement these equations.

Sol.)

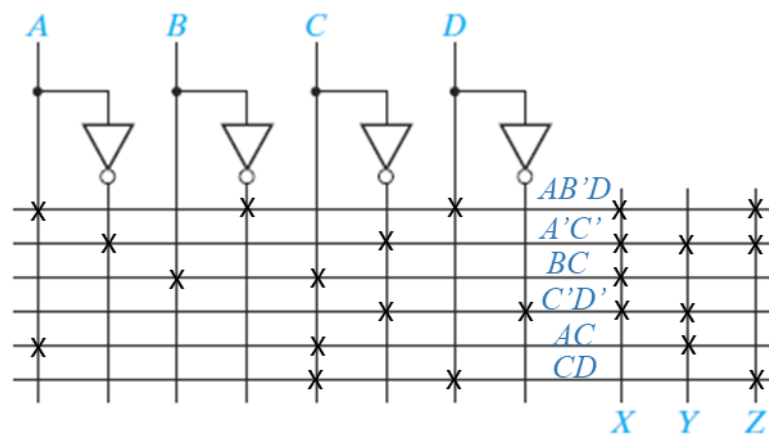

(b) Specify the truth table for a ROM which realizes these same equations.

Sol.)

A B C D	X Y Z
0 0 0 0	1 1 1
0 0 0 1	1 1 1
0 0 1 0	0 0 0
0 0 1 1	0 0 1
0 1 0 0	1 1 1
0 1 0 1	1 1 1
0 1 1 0	1 0 0
0 1 1 1	1 0 1
1 0 0 0	1 1 0
1 0 0 1	1 0 1
1 0 1 0	0 1 0
1 0 1 1	1 1 1
1 1 0 0	1 1 0
1 1 0 1	0 0 0
1 1 1 0	1 1 0
1 1 1 1	1 1 1

2. A U-V flip-flop behaves as follows:

If $UV = 00$, the flip-flop does not change state.

If $UV = 10$, the flip-flop is set to $Q = 0$.

If $UV = 11$, the flip-flop changes states.

The input combination $UV = 01$ is not allowed.

(a) Give the characteristic (next state) equation for this flip-flop.

Sol.)

Q	UV = 00	UV = 01	UV = 11	UV = 10
0	0	x	1	0
1	1	x	0	0

$$Q^+ = U'Q + VQ'$$

UV \ Q	0	1
	Q	Q'
00	0	1
01	X	X
11	1	0
10	0	0

(b) Complete the following table, using don't-cares where possible.

(Sol.)

Q Q ⁺	UV
00	x 0
01	1 1
10	1 x
11	0 0

(c) Realize the following next-state equation for Q using a U-V flip-flop: $Q^+ = A + BQ$. Find equations for U and V.

Sol.)

Q	Q ⁺			
	AB = 00	AB = 01	AB = 11	AB = 10
0	0	0	1	1
1	0	1	1	1

Q	U V			
	AB = 00	AB = 01	AB = 11	AB = 10
0	x0	x0	11	11
1	1x	00	00	00

$$U = A'B' + Q'$$

$$V = AQ'$$

AB \ Q	0	1
	U	V
00	X	1
01	X	0
11	1	0
10	1	0

3. Design a 3-bit counter which counts in the sequence:

001, 100, 101, 111, 110, 010, 011, (repeat) 001, ...

Sol.)

ABC	$A^+B^+C^+$
000	X X X
001	1 0 0
010	0 1 1
011	0 0 1
100	1 0 1
101	1 1 1
110	0 1 0
111	1 1 0

TABLE 12-9
Determination of
Flip-Flop Input
Equations from
Next-State
Equations
Using Karnaugh
Maps
© Cengage Learning 2014

Type of Flip-Flop	Input	$Q = 0$		$Q = 1$		Rules for Forming Input Map From Next-State Map*	
		$Q^+ = 0$	$Q^+ = 1$	$Q^+ = 0$	$Q^+ = 1$	$Q = 0$ Half of Map	$Q = 1$ Half of Map
Delay	D	0	1	0	1	no change	no change
Toggle	T	0	1	1	0	no change	complement
Set-Reset	S	0	1	0	X	no change	replace 1's with X's**
	R	X	0	1	0	replace 0's with X's**	complement
J-K	J	0	1	X	X	no change fill in with X's	fill in with X's
	K	X	X	1	0		complement

Q^+ means the next state of Q

X is a don't-care

*Always copy X's from the next-state map onto the input maps first.

**Fill in the remaining squares with 0's.

(a) Use D flip-flops.

Sol.)

BC		A	
		0	1
00	00	X	1
01	01	1	1
11	11	0	1
10	10	0	0

A^+

BC		A	
		0	1
00	00	X	0
01	01	0	1
11	11	0	1
10	10	1	1

B^+

BC		A	
		0	1
00	00	X	1
01	01	0	1
11	11	1	0
10	10	1	0

C^+

$$D_A = B' + AC; D_B = AC + BC'; D_C = A'B + AB'$$

(b) Use J-K flip-flops.

Sol.)

BC		A	
		0	1
00	00	X	X
01	01	1	X
11	11	0	X
10	10	0	X

J_A

BC		A	
		0	1
00	00	X	0
01	01	X	0
11	11	X	0
10	10	X	1

K_A

BC		A	
		0	1
00	00	X	0
01	01	0	1
11	11	X	1
10	10	X	X

J_B

BC		A	
		0	1
00	00	X	X
01	01	X	X
11	11	1	0
10	10	0	0

K_B

BC		A	
		0	1
00	00	X	1
01	01	X	X
11	11	X	X
10	10	1	0

J_C

BC		A	
		0	1
00	00	X	X
01	01	1	0
11	11	0	1
10	10	X	X

K_C

$$J_A = B', K_A = BC'; J_B = AC, K_B = A'C; J_C = A' + B', K_C = A'B' + AB$$

(c) Use T flip-flops.

Sol.)

		A	
		0	1
BC	00	X	0
	01	1	0
	11	0	0
	10	0	1

A^+

		A	
		0	1
BC	00	X	0
	01	0	1
	11	1	0
	10	0	0

B^+

		A	
		0	1
BC	00	X	1
	01	1	0
	11	0	1
	10	1	0

C^+

$$T_A = A'B' + ABC'; T_B = A'BC + AB'C; T_C = A'B' + A'C' + B'C' + ABC$$

(d) Use S-R flip-flops.

Sol.)

		A	
		0	1
BC	00	X	X
	01	1	X
	11	0	X
	10	0	0

S_A

		A	
		0	1
BC	00	X	0
	01	0	0
	11	X	0
	10	X	1

R_A

		A	
		0	1
BC	00	X	0
	01	0	1
	11	0	X
	10	X	X

S_B

		A	
		0	1
BC	00	X	X
	01	X	0
	11	1	0
	10	0	0

R_B

		A	
		0	1
BC	00	X	1
	01	0	X
	11	X	0
	10	1	0

S_C

		A	
		0	1
BC	00	X	0
	01	1	0
	11	0	1
	10	0	X

R_C


$$S_A = B', R_A = BC'; S_B = AC, R_B = A'C; S_C = A'B + AB', R_C = A'B' + AB$$

(e) What will happen if the counter of (a) is started in state 000?

Sol.)

State 000 goes to 100, because $D_A D_B D_C = 100$.

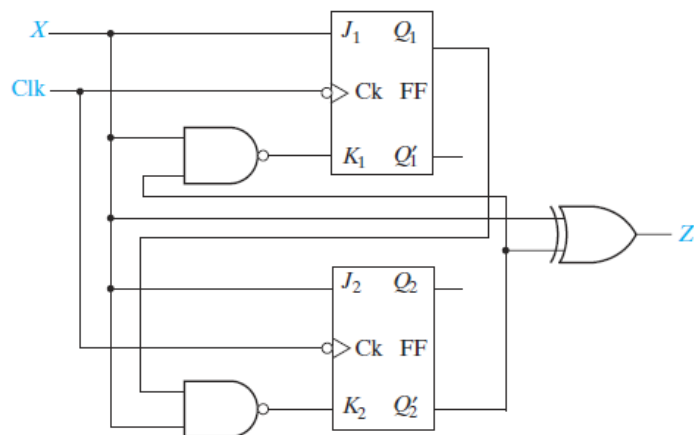4. (a) Construct a transition table and state graph for the circuit shown below.




Sol.)

$$Q_1^+ = J_1 Q_1' + K_1' Q_1 = X Q_1' + X Q_2' Q_1$$

$$Q_2^+ = J_2 Q_2' + K_2' Q_2 = X Q_2' + X Q_1 Q_2$$


$$Z = X' Q_2' + X Q_2$$

Present State $Q_1 Q_2$	Next State $Q_1^+ Q_2^+$		Z	
	$X=0$	$X=1$	$X=0$	$X=1$
00	00	11	1	0
01	00	10	0	1
11	00	01	0	1
10	00	11	1	0

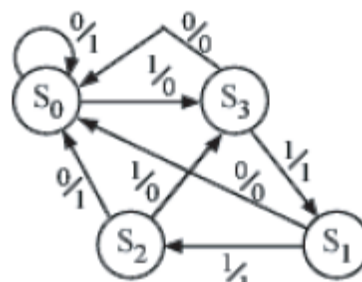

- (b) Construct a timing chart for the circuit for an input sequence $X = 10111$. (Assume that initially $Q_1 = Q_2 = 0$ and that X changes midway between the rising and falling clock edges.)

(Sol.)

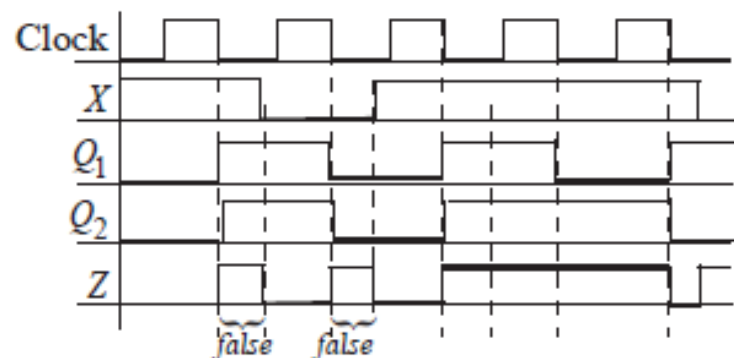

- (c) List the output values produced by the input sequence.

Sol.) $Z = 00011$