

Name _____ Student ID _____ Colleges & Schools _____ Department _____

Pretest


1. The following PLA will be used to implement the following equations:

$$X = AB'D + A'C' + BC + C'D'$$

$$Y = A'C' + AC + C'D'$$

$$Z = CD + A'C' + AB'D$$

 (a) Indicate the connections that will be made to program the PLA to implement these equations.



(b) Specify the truth table for a ROM which realizes these same equations.

2. A U-V flip-flop behaves as follows:

If $UV = 00$, the flip-flop does not change state.

If $UV = 10$, the flip-flop is set to $Q = 0$.

If $UV = 11$, the flip-flop changes states.

The input combination $UV = 01$ is not allowed.

(a) Give the characteristic (next state) equation for this flip-flop.

(b) Complete the following table, using don't-cares where possible.

Q	Q^+	U	V
0	0		
0	1		
1	0		
1	1		

(c) Realize the following next-state equation for Q using a U-V flip-flop: $Q^+ = A + BQ$. Find equations for U and V .

3. Design a 3-bit counter which counts in the sequence:

001, 100, 101, 111, 110, 010, 011, (repeat) 001, ...

(a) Use D flip-flops.


(b) Use J-K flip-flops.

(c) Use T flip-flops.

(d) Use S-R flip-flops.

(e) What will happen if the counter of (a) is started in state 000?

 4. (a) Construct a transition table and state graph for the circuit shown below.



(b) Construct a timing chart for the circuit for an input sequence $X = 10111$. (Assume that initially $Q_1 = Q_2 = 0$ and that X changes midway between the rising and falling clock edges.)

(c) List the output values produced by the input sequence.