

Name _____ Student ID _____ Colleges & Schools _____ Department _____


Homework Unit 4 Solutions

1. A combinational logic circuit has four inputs (A , B , C , and D) and one output Z . The output is 1 iff the input has three consecutive 0's or three consecutive 1's. For example, if $A=1$, $B=0$, $C=0$, and $D=0$, then $Z=1$, but if $A=0$, $B=1$, $C=0$, and $D=0$, then $Z=0$. Design the circuit using one four-input OR gate and four three-input AND gates.

Sol.)

$A B C D$	Z
0 0 0 0	1
0 0 0 1	1
0 0 1 0	0
0 0 1 1	0
0 1 0 0	0
0 1 0 1	0
0 1 1 0	0
0 1 1 1	1
1 0 0 0	1
1 0 0 1	0
1 0 1 0	0
1 0 1 1	0
1 1 0 0	0
1 1 0 1	0
1 1 1 0	1
1 1 1 1	1
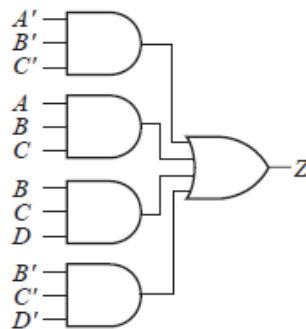
$$\begin{aligned}
 Z &= A'B'C'D' + A'B'C'D + AB'C'D' \\
 &\quad + ABCD' + ABCD + A'BCD \\
 &= A'B'C' + ABC + AB'C'D' + A'BCD \\
 &= A'B'C' + ABC + AB'C'D' + A'BCD + \underline{BCD} + \underline{B'C'D'} \\
 &\quad \text{(Added consensus terms)} \\
 \therefore Z &= A'B'C' + ABC + BCD + B'C'D'
 \end{aligned}$$



2. Given $F_1 = \prod M(0, 4, 5, 6)$ and $F_2 = \prod M(0, 4, 7)$, find the maxterm expansion for $F_1 F_2$. State a general rule for finding the maxterm expansion of $F_1 F_2$ given the maxterm expansions of F_1 and F_2 . Prove your answer by using the general form of the maxterm expansion.

Sol.) $F_1 F_2 = \prod M(0, 4, 5, 6, 7)$. General rule: $F_1 F_2$ is the product of all maxterms that are not present in either F_1 or F_2 .

Proof: Let $F_1 = \prod (a_i + M_i)$; $F_2 = \prod (b_j + M_j)$;

$$\begin{aligned}
 F_1 F_2 &= \prod (a_i + M_i) \prod (b_j + M_j) = (a_0 + M_0) (b_0 + M_0) (a_1 + M_1) (b_1 + M_1) \cdots \\
 &= (a_0 b_0 + M_0) (a_1 b_1 + M_1) (a_2 b_2 + M_2) \cdots = \prod (a_i b_i + M_i)
 \end{aligned}$$

Maxterm M_i is present in $F_1 F_2$ iff $a_i b_i = 0$, i.e., if either $a_i = 0$ or $b_i = 0$. Maxterm M_i is present

in F_1 iff $a_i = 0$. Maxterm M_i is present in F_2 iff $b_i = 0$. Therefore, maxterm M_i is present in $F_1 F_2$

iff it is present in F_1 or F_2 .

3. Given $f(a, b, c) = a(b+c')$.

Sol.) $f(a,b,c) = a(b+c') = ab+ac' = ab(c+c') + a(b+b')c' = abc + abc' + abc' + ab'c'$.

$$= abc + abc' + ab'c' = m_7 + m_6 + m_4.$$

- (a) Express f as a minterm expansion (use m -notation).

$$\text{Sol.) } f = \sum m(4, 6, 7)$$

- (b) Express f as a maxterm expansion (use M -notation).

$$\text{Sol.) } f = \prod M(0, 1, 2, 3, 5)$$

- (c) Express f' as a minterm expansion (use m -notation).

$$\text{Sol.) } f' = \sum m(0, 1, 2, 3, 5)$$

- (d) Express f' as a maxterm expansion (use M -notation).

$$\text{Sol.) } f' = \prod M(4, 6, 7)$$

4. (a) If m_1 and m_2 are minterms of n variables, prove that $m_1+m_2 = m_1 \oplus m_2$.

$$\text{Sol.) } m_1+m_2 = m_1(m_2'+m_2)+(m_1'+m_1)m_2 = m_1m_2'+m_1m_2+m_1'm_2$$

$$\text{But } m_1m_2 = 0, \text{ so } m_1+m_2 = m_1m_2'+m_1'm_2 = m_1 \oplus m_2.$$

- (b) Prove that any switching function can be written as the exclusive OR sum of products where each product does not contain a complemented literal. (*Hint*: Start with the function written as a sum of minterms and use part (a).)

Sol.) Using part (a), any function can be written as the exclusive OR sum of its minterms.

However, if a product contains a complemented literal, it can be written as the exclusive OR sum of two products without a complemented literal by using

$$x'p = (x \oplus 1)p = xp \oplus p.$$

By repeated application of the preceding relationship, all complemented literals can be removed from the products.