

Name _____ Student ID _____ Colleges & Schools _____ Department _____

Quiz Unit 12

1. A 74178 shift register is described by the given table. All state changes occur on the 1-0 transition of the clock. The shift register is connected as shown. Complete the timing diagram.

