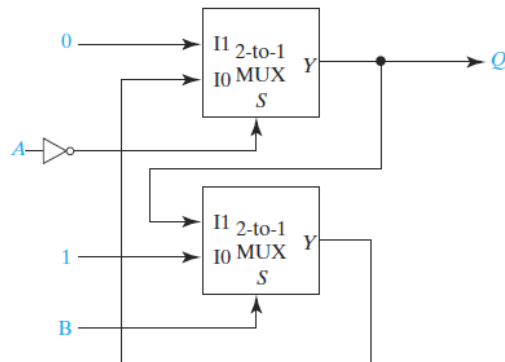


Name \_\_\_\_\_ Student ID \_\_\_\_\_ Colleges & Schools \_\_\_\_\_ Department \_\_\_\_\_

### Homework Unit 11 Solutions

1. Analyze the latch circuit shown below.



- (a) Construct a state table for this circuit and identify the stable states of the circuit.

Sol.) A state table is shown below and the circle represents the stable states.

Present State $Q$	Next State $Q^+$			
	$AB$ 0 0	$AB$ 0 1	$AB$ 1 1	$AB$ 1 0
0	0	0	0	1
1	0	0	1	1


- (b) Derive a Boolean algebra equation for the next value of the output  $Q$  in terms of  $Q$ ,  $A$  and  $B$ .

Sol.)  $Q^+ = A(B' + Q)$

- (c) Analyze the behavior of the circuit. Is it a useful circuit?

Sol.) This is a reset dominant latch where  $A'$  acts a reset and  $B'$  acts as a set.

 
2. Complete the following diagrams for the rising-edge-triggered D flip-flop shown below.




- (a) First draw  $Q$  based on the behavior of a D flip-flop.

- (b) Draw in the internal signal  $P$ .

Sol.)

 


 3. The ClrN and PreN inputs are called asynchronous because they operate independently of the clock (i.e., they are not synchronized with the clock). We can also make flip-flops with synchronous clears or preset inputs. A D-flip-flop with an active-low synchronous ClrN input may be constructed from a regular D flip-flop as follows.




Fill in the timing diagram. For  $Q_1$ , assume a synchronous ClrN as in Figure (a), and for  $Q_2$ , assume an asynchronous ClrN as in Figure (b). Assume  $Q_1 = Q_2 = 0$  at the beginning.

Sol.)

 

 4. (a) Construct a D flip-flop using an inverter and an S-R flip-flop. (Hint: When  $D = 0$ ,  $Q^+ = 0$ , and when  $D = 1$ ,  $Q^+ = 1$ , i.e.,  $Q^+ = D$ )



Sol.) When  $D = 0$ , then  $S = 0$ ,  $R = 1$ , so  $Q^+ = 0$ .

When  $D = 1$ , then  $S = 1$ ,  $R = 0$ , so  $Q^+ = 1$ .

(b) If the propagation delay and setup time of the S-R flip-flop in (a) are 2.5ns and 1.5ns, respectively, and if the inverter has a propagation delay of 1ns, what are the propagation delay and setup time of the D flip-flop of part (a)?

Sol.)

R will not be ready until D goes through the inverter, so we must add the delay of the inverter to the setup time. Thus, Setup time =  $1.5 + 1 = 2.5$ ns.

Propagation delay for the D flip-flop is 2.5ns which is same as for the S-R flip-flop, since the propagation delay is measured with respect to the clock.