


Name _____ Student ID _____ Colleges & Schools _____ Department _____

Homework Unit 12 Solutions

- Construct a 4-bit Johnson counter using J-K flip-flops. What sequence of states does the counter go through if it is started in state 0000? State 0110?


(Hint: refer a 3-bit Johnson counter shown below)

FIGURE 12-12
Shift Register
with Inverted
Feedback
© Cengage Learning 2014

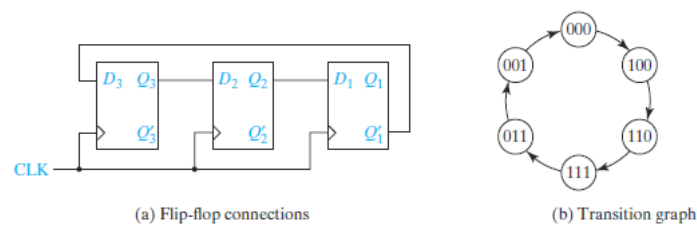

Sol.)

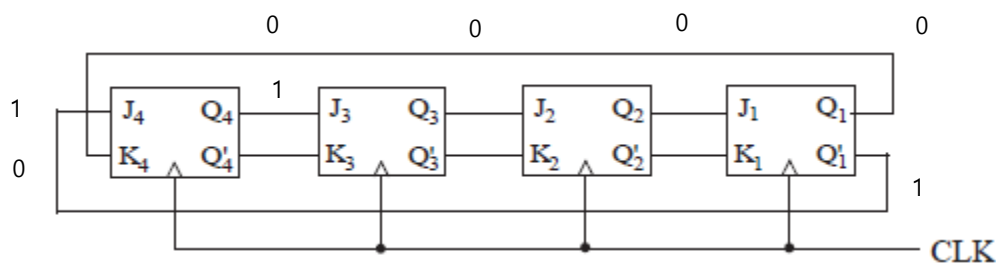4-bit Johnson counter using J-K flip-flops:



Starting in 0000: 0000, 1000, 1100, 1110, 1111, 0111, 0011, 0001, (repeat) 0000, ...

Starting in 0110: 0110, 1011, 0101, 0010, 1001, 0100, 1010, 1101, (repeat) 0110, ...

2. Design a 3-bit counter using D flip-flops which counts in the sequence: 001, 100, 101, 111, 110, 010, 011, (repeat) 001, ... What will happen if the counter is started in state 000?

Sol.) A transition table for this binary counter can be represented as

$A B C$	$A^+ B^+ C^+$
0 0 0	X X X
0 0 1	1 0 0
0 1 0	0 1 1
0 1 1	0 0 1
1 0 0	1 0 1
1 0 1	1 1 1
1 1 0	0 1 0
1 1 1	1 1 0

BC \ A		0	1
		A^+	
00		X	1
01		1	1
11		0	1
10		0	0

BC \ A		0	1
		B^+	
00		X	0
01		0	1
11		0	1
10		1	1

BC \ A		0	1
		C^+	
00		X	1
01		0	1
11		1	0
10		1	0

$$D_A = B' + AC;$$

$$D_B = AC + BC';$$

$$D_C = A'B + AB'$$

→ State 000 goes to 100, because $D_A D_B D_C = 100$

3. A sequential circuit contains a register of four flip-flops. Initially a binary number N ($0000 \leq N \leq 1100$) is stored in the flip-flops. After a single clock pulse is applied to the circuit, the register should contain $N + 0011$. In other words, the function of the sequential circuit is to add 3 to the contents of a 4-bit register. Design the circuit using J-K flip-flops.

Sol.) A transition table for a given sequential circuit can be expressed as

$ABCD$	$A^*B^*C^*D^*$	$J_A K_A J_B K_B J_C K_C J_D K_D$
0000	0011	0 X 0 X 1 X 1 X
0001	0100	0 X 1 X 0 X X 1
0010	0101	0 X 1 X X 1 1 X
0011	0110	0 X 1 X X 0 X 1
0100	0111	0 X X 0 1 X 1 X
0101	1000	1 X X 1 0 X X 1
0110	1001	1 X X 1 X 1 1 X
0111	1010	1 X X 1 X 0 X 1
1000	1011	X 0 0 X 1 X 1 X
1001	1100	X 0 1 X 0 X X 1
1010	1101	X 0 1 X X 1 1 X
1011	1110	X 0 1 X X 0 X 1
1100	1111	X 0 X 0 1 X 1 X
1101	XXXX	X X X X X X X
1110	XXXX	X X X X X X X
1111	XXXX	X X X X X X X

AB CD		J_A			
		00	01	11	10
00	0	0	X	X	
01	0	1	X	X	
11	0	1	X	X	
10	0	1	X	X	

AB CD		K_A			
		00	01	11	10
CD	00	X	X	0	0
	01	X	X	X	0
	11	X	X	X	0
	10	X	X	X	0

AB CD		00	01	11	10
		0	X	X	0
J_B	00	0	X	X	0
	01	1	X	X	1
	11	1	X	X	1
	10	1	X	X	1

AB CD		K_B			
		00	01	11	10
00	X	0	0	X	
01	X	1	X	X	
11	X	1	X	X	
10	X	1	X	X	

AB	00	01	11	10	
CD	00	1	1	1	1
	01	0	0	X	0
	11	X	X	X	X
	10	X	X	X	X

J_C

AB	00	01	11	10	
CD	00	X	X	X	X
	01	X	X	X	X
	11	0	0	X	0
	10	1	1	X	1

K_C

AB CD		00	01	11	10
		00	01	11	10
J_D	00	1	1	1	1
	01	X	X	X	X
	11	X	X	X	X
	10	1	1	X	1

AB	00	01	11	10	
CD	00	X	X	X	X
	01	1	1	1	X
	11	1	1	1	X
	10	X	X	X	X

K_D

Using Karnaugh maps:

$$J_A = A + BD + BC, K_A = 0$$

$$J_B = C + D, K_B = C + D$$

$$J_C = D', K_C = D'$$

$$J_D = 1, K_D = 1$$

4. An L-M flip-flop works as follows:

If $LM = 00$, the next state of the flip-flop is 1.

If $LM = 01$, the next state of the flip-flop is the same as the present state.

If $LM = 10$, the next state of the flip-flop is the complement of the present state.

If $LM = 11$, the next state of the flip-flop is 0.

(a) Complete the following table (use don't-cares when possible).

Sol.)

$Q Q^*$	LM
0 0	$\begin{matrix} 0 1 \\ 1 1 \end{matrix} \} X1$
0 1	$\begin{matrix} 0 0 \\ 1 0 \end{matrix} \} X0$
1 0	$\begin{matrix} 1 0 \\ 1 1 \end{matrix} \} 1X$
1 1	$\begin{matrix} 0 0 \\ 0 1 \end{matrix} \} 0X$

(b) Using this table and Karnaugh maps, derive and minimize the input equations for a counter composed of three L-M flip-flops which counts in the following sequence: $ABC = 000, 100, 101, 111, 011, 001$, (repeat) $000, \dots$

Sol.) $L_A = B$, $M_A = C$; $L_B = A'$, $M_B = A' + C'$; $L_C = A'B'$, $M_C = A'$;

ABC	$A^*B^*C^*$
000	100
001	000
010	XXX
011	001
100	101
101	111
110	XXX
111	011

A^*	A	B	C
00	0	1	1
01	0	1	0
11	0	0	0
10	X	X	X

B^*	A	B	C
00	0	0	0
01	0	0	1
11	0	1	1
10	X	X	X

C^*	A	B	C
00	0	0	1
01	0	0	1
11	1	1	1
10	X	X	X

A	B	C
00	X	0
01	X	0
11	X	1
10	X	X

$$L_A = B$$

A	B	C
00	0	X
01	1	X
11	1	X
10	X	X

$$M_A = C$$

A	B	C
00	0	X
01	X	X
11	1	0
10	X	X

$$L_B = A'$$

A	B	C
00	1	1
01	1	0
11	X	X
10	X	X

$$M_B = A' + C'$$

A	B	C
00	0	X
01	1	0
11	0	0
10	X	X

$$L_C = A'B'$$

A	B	C
00	1	0
01	X	X
11	X	X
10	X	X

$$M_C = A'$$