

Boolean Algebra I

Contents

1. Introduction
2. Basic Operations
3. Boolean Expressions and Truth Tables
4. Basic Theorems
5. Commutative, Associative, Distributive and DeMorgan's Laws
6. Simplification Theorems
7. Multiplying Out and Factoring
8. Complementing Boolean Expressions

Objectives


- Understand the basic operations and laws of Boolean algebra.
- Relate these operations and laws to circuits composed of AND gates, OR gates, INVERTERS and switches.
- Prove any of these laws in switching algebra using a truth table.
- Apply these laws to the manipulation of algebraic expressions including: obtaining a sum of products or product of sums, simplifying an expression and/or finding the complement of an expression

Introduction


- All switching devices we will use are two-state devices, so we will emphasize the case in which all variables assume only one of two values.
- Boolean variable X or Y will be used to represent input or output of switching circuit.
- Symbols “0” and “1” represent the two values any variable can take on. These represent states in a logic circuit, and do not have numeric value.
- **Logic gate:** 0 usually represents range of low voltages and 1 represents range of high voltages
- **Switch circuit:** 0 represents open switch and 1 represents closed switch
- 0 and 1 can be used to represent the two states in any binary valued system.

Boole/Shannon/Shockley


- Basic mathematics needed for logic design of digital systems is Boolean algebra.
- George Boole developed Boolean algebra in 1847 and used it to solve problems in mathematical logic.
- Two-valued Boolean algebra is often called *switching algebra*.
- Claude Shannon first applied Boolean algebra to the design of switching circuits in 1939.
- In 1947, William Shockley invented the first transistor.

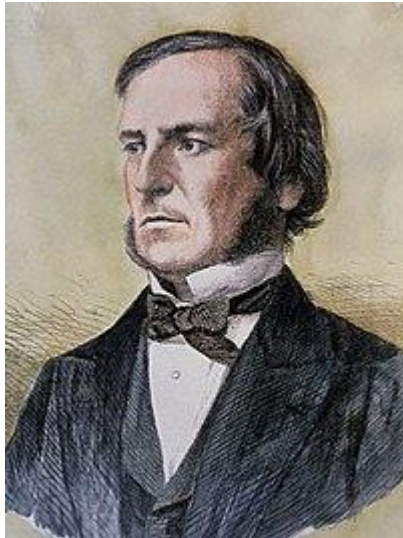

George Boole (1815~1864)

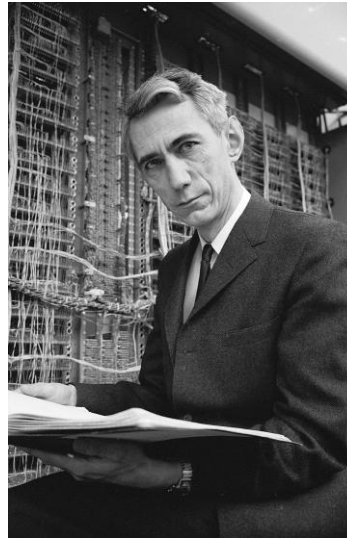

Claude Shannon (1916~2001)

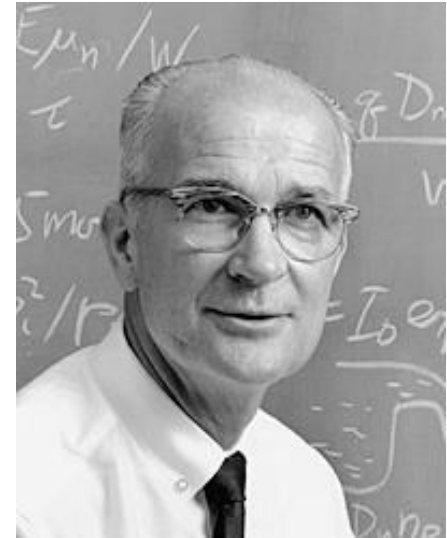


William Bradford Shockley Jr. (1910~1989)


Basic Operations

Basic Operations:

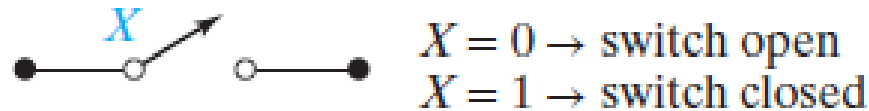- The basic operations of Boolean (switching) algebra are called **AND**, **OR**, and **Complement (or Inverse)**.
- To apply switching algebra to a switch circuit, each switch contact is labeled with a variable.



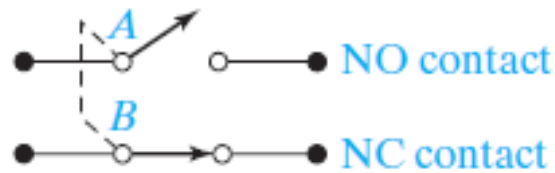- NC (normally closed) and NO (normally open) contacts are always in opposite states.





- If variable X is assigned to NO contact, then X' will be assigned for NC.

Basic Operations

Complementation / Inversion:

- Prime (') denotes complementation, i.e., $0' = 1$ and $1' = 0$
- For a switching variable, X :
 - ✓ $X' = 1$ if $X = 0$ and $X' = 0$ if $X = 1$
- Complementation is also called inversion. An inverter is represented as shown below, where circle (bubble) at the output denotes inversion:
- Figure A-4(b) shows CMOS (Complementary Metal Oxide Semiconductor) inverter. The switch analog in Figure A-4(c) illustrates the operation of the inverter when the inverter input is 0. Q_1 is on and Q_2 is off as indicated by the closed and open switches. When the input is $+V$ (logic 1), Q_1 is off and Q_2 is on, as indicated by the open and closed switches in Figure A-4(d). The following table summarizes the operation:

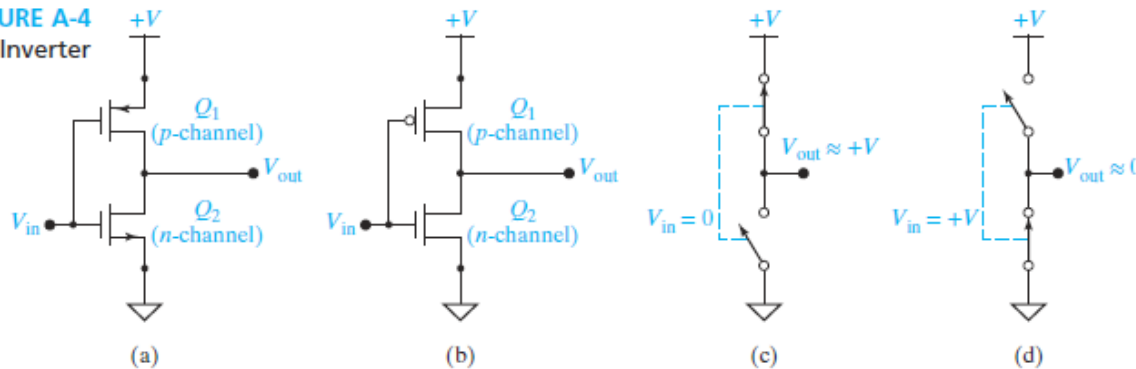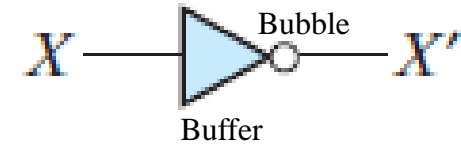

V_{in}	V_{out}	Q_1	Q_2
0	$+V$	ON	OFF
$+V$	0	OFF	ON

© Cengage Learning 2014

Basic Operations



Series Switching Circuits / AND operation:

- A) Truth table B) Logic gate diagram
C) Switch circuit diagram

- The operation defined by the table is called AND.
- It is written algebraically as $C = A \cdot B$.
- We will usually write AB instead of $A \cdot B$.
- The AND operation is also referred to as logical (or Boolean) multiplication.

A)

A	B	$C = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

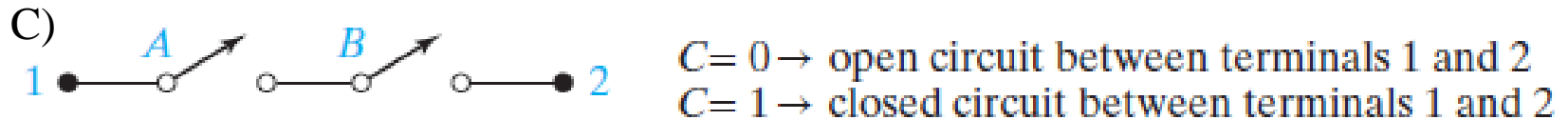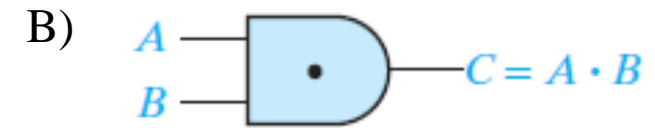

- When switch contacts A and B are connected in series, there is an open circuit between the terminals if either A or B or both are open (0), and there is a closed circuit between the terminals only if both A and B are closed (1).

Basic Operations

Parallel Switching Circuits / OR operation:



- A) Truth table B) Logic gate diagram
C) Switch circuit diagram

- The operation defined by the table is called OR.
- It is written algebraically as $C=A+B$.
- The OR operation is also referred to as logical (or Boolean) addition.

If switches A and B are connected in parallel, there is a closed circuit if either A or B , or both, are closed and an open circuit only if A and B are both open.

A)

A	B	$C = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

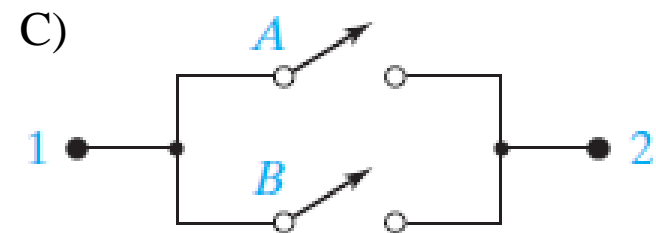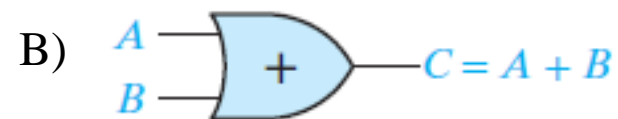

Boolean Expressions and Truth Tables

Examples of Boolean Expressions and Corresponding Diagrams:



- Expressions

$$AB' + C \quad (2-1)$$

$$[A(C + D)]' + BE \quad (2-2)$$

- Order of operations- Parentheses, Inversion, AND, OR

- Logic Diagrams

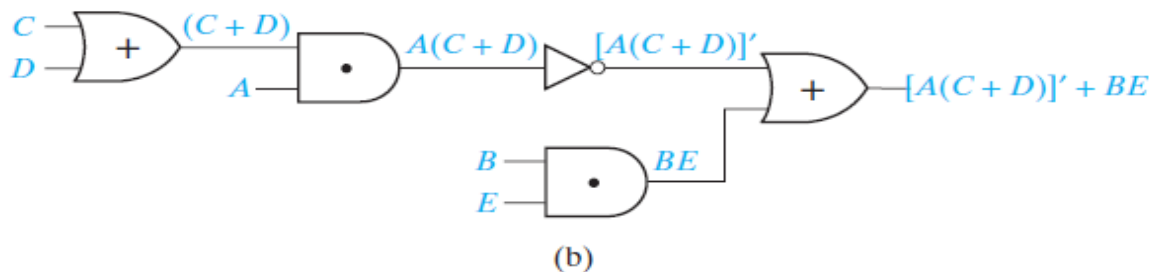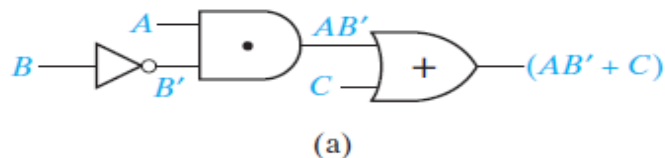

- The following expression

$$ab'c + a'b + a'bc' + b'c'$$

has 3 variables (a , b , and c) and 10 literals.


Boolean Expressions and Truth Tables

Truth Tables:

A truth table specifies the values of a Boolean expression for every possible combination of values of the variables in the expression.

FIGURE 2-2
Two-Input Circuit
and Truth Table

© Cengage Learning 2014

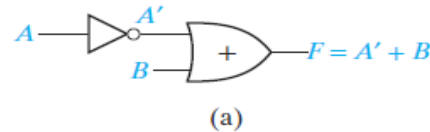

(b)

A	B	A'	F = A' + B
0	0	1	1
0	1	1	1
1	0	0	0
1	1	0	1

Equal Boolean Expressions:

Two Boolean expressions are said to be **equal** if they have the same value for every possible combination of the variables.

TABLE 2-1

© Cengage Learning 2014

A	B	C	B'	AB'	AB' + C	A + C	B' + C	(A + C)(B' + C)
0	0	0	1	0	0	0	1	0
0	0	1	1	0	1	1	1	1
0	1	0	0	0	0	0	0	0
0	1	1	0	0	1	1	1	1
1	0	0	1	1	1	1	1	1
1	0	1	1	1	1	1	1	1
1	1	0	0	0	0	1	0	0
1	1	1	0	0	1	1	1	1

$$AB' + C = (A + C)(B' + C) \quad (2-3)$$

An n -variable expression will have 2^n rows in its truth table.

Basic Theorems

Single Variable Basic Theorems:

- The following basic laws and theorems of Boolean algebra involve only a single variable:

Operations with 0 and 1:

$$X + 0 = X \quad (2-4) \qquad X \cdot 1 = X \quad (2-4D)$$

$$X + 1 = 1 \quad (2-5) \qquad X \cdot 0 = 0 \quad (2-5D)$$

Idempotent laws:

$$X + X = X \quad (2-6) \qquad X \cdot X = X \quad (2-6D)$$

Involution law:

$$(X')' = X \quad (2-7)$$

Laws of complementarity:

$$X + X' = 1 \quad (2-8) \qquad X \cdot X' = 0 \quad (2-8D)$$

- Any expression can be substituted for the variable X in these theorems.

$$\begin{aligned} (AB+D)E + 1 &= 1 && \text{from (2-5)} \\ (AB'+D)(AB'+D)' &= 0 && \text{from (2-5D)} \end{aligned}$$

Commutative, Associative, Distributive, and DeMorgan's Law

Commutative and Associative Laws:

Commutative: Order in which variables are written does not affect result of applying AND and OR operations.

$$XY = YX \quad (2-9) \quad \text{and} \quad X+Y = Y+X \quad (2-9D)$$

Associative: Result of AND and OR operations is independent of which variables we associate together first.

$$(XY)Z = X(YZ) = XYZ \quad (2-10)$$

$$(X+Y)+Z = X+(Y+Z) = X+Y+Z \quad (2-10D)$$

Commutative, Associative, Distributive, and DeMorgan's Law

Distributive Law:

Distributive: The distributive law of Boolean algebra is as follows:

$$X (Y + Z) = XY + XZ$$

Furthermore, a **second distributive law** is valid for Boolean algebra but not ordinary algebra and very useful in manipulating Boolean expressions.

$$X + YZ = (X + Y)(X + Z)$$

Proof of a second distributed law:

$$\begin{aligned}(X + Y)(X + Z) &= X(X+Z) + Y(X+Z) = XX + XZ + YX + YZ \\&= X + XZ + XY + YZ = X \cdot 1 + XZ + XY + YZ \\&= X(1+Z+Y) + YZ = X \cdot 1 + YZ \\&= X + YZ\end{aligned}$$

This second law is very useful in manipulating Boolean expressions.

Commutative, Associative, Distributive, and DeMorgan's Law

DeMorgan's Law:

DeMorgan's Law is stated as follows:

$$(X + Y)' = X'Y'$$

$$(XY)' = X' + Y'$$

Truth table proof of DeMorgan's Laws is shown below:

X	Y	X'	Y'	$X + Y$	$(X + Y)'$	$X'Y'$	XY	$(XY)'$	$X' + Y'$
0	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	0	0	1	1
1	0	0	1	1	0	0	0	1	1
1	1	0	0	1	0	0	1	0	0

Commutative, Associative, Distributive, and DeMorgan's Law

Laws of Boolean Algebra:

Operations with 0 and 1:

1. $X + 0 = X$

2. $X + 1 = 1$

1D. $X \cdot 1 = X$

2D. $X \cdot 0 = 0$

Idempotent laws:

3. $X + X = X$

3D. $X \cdot X = X$

Involution law:

4. $(X')' = X$

Laws of complementarity:

5. $X + X' = 1$

5D. $X \cdot X' = 0$

Commutative laws:

6. $X + Y = Y + X$

6D. $XY = YX$

Associative laws:

7. $(X + Y) + Z = X + (Y + Z)$
 $= X + Y + Z$

7D. $(XY)Z = X(YZ) = XYZ$

Distributive laws:

8. $X(Y + Z) = XY + XZ$

8D. $X + YZ = (X + Y)(X + Z)$

DeMorgan's laws:

9. $(X + Y)' = X'Y'$

9D. $(XY)' = X' + Y'$

Simplification Theorems

Simplification Theorems:

- Theorems used to replace an expression with a simpler expression are called **simplification theorems**.

Uniting theorems:

1. $XY + XY' = X$

1D. $(X + Y)(X + Y') = X$

Absorption theorems:

2. $X + XY = X$

2D. $X(X + Y) = X$

Elimination theorems:

3. $X + X'Y = X + Y$

3D. $X(X' + Y) = XY$

Duality:

4. $(X + Y + Z + \dots)^D = XYZ \dots$

4D. $(XYZ \dots)^D = X + Y + Z + \dots$

Theorems for multiplying out and factoring:

5. $(X + Y)(X' + Z) = XZ + X'Y$

5D. $XY + X'Z = (X + Z)(X' + Y)$

Consensus theorems:

6. $XY + YZ + X'Z = XY + X'Z$

6D. $(X + Y)(Y + Z)(X' + Z) = (X + Y)(X' + Z)$

Simplification Theorems

Proof of Simplification Theorems:

- Using switching algebra, the theorems on the previous slide can be proven using truth tables.
- In general Boolean algebra, these theorems must be proven algebraically starting with basic theorems.

Proof of (2-15): $XY + XY' = X(Y + Y') = X(1) = X$

Proof of (2-16): $X + XY = X \cdot 1 + XY = X(1 + Y) = X \cdot 1 = X$

Proof of (2-17): $X + X'Y = (X + X')(X + Y) = 1(X + Y) = X + Y$

Proof of (2-18): $XY + X'Z + YZ = XY + X'Z + (1)YZ =$
 $XY + X'Z + (X + X')YZ = XY + XYZ + X'Z + X'YZ =$
 $XY + X'Z$ (using absorption twice)

$$(X+Y)(Y+Z)(X'+Z) = (X+Y)(XX'+Y+Z)(X'+Z) =$$
$$(X+Y+0)(X+Y+Z)(X'+Y+Z)(X'+0+Z) =$$
$$(X+Y+0 \cdot Z)(X'+0 \cdot Y+Z) = (X+Y)(X'+Z)$$

Multiplying Out and Factoring

Sum of Product:

An expression is said to be in *sum-of-products* (SOP) form when all products are the products of single variables. This form is the end result when an expression is fully multiplied out.

For example:

$$AB' + CD'E + AC'E'$$

$$ABC' + DEFG + H$$

Product of Sum:

An expression is in *product-of-sums* (POS) form when all sums are the sums of single variables. It is usually easy to recognize a product-of-sums expression since it consists of a product of sum terms.

For example:

$$(A + B')(C + D' + E)(A + C' + E')$$

$$(A + B)(C + D + E)F$$

Multiplying Out and Factoring

Examples: Factoring using the distributed law

Example 1

Factor $A + B'CD$. This is of the form $X + YZ$ where $X = A$, $Y = B'$, and $Z = CD$, so

$$A + B'CD = (X + Y)(X + Z) = (A + B')(A + CD)$$

$A + CD$ can be factored again using the second distributive law, so

$$A + B'CD = (A + B')(A + C)(A + D)$$

Example 2

Factor $AB' + C'D$.

$$AB' + C'D = (AB' + C')(AB' + D) \quad \leftarrow \text{note how } X + YZ = (X + Y)(X + Z) \text{ was applied here}$$

$$= (A + C')(B' + C')(A + D)(B' + D) \quad \leftarrow \text{the second distributive law was applied again to each term}$$

Complementing Boolean Expressions

Using DeMorgan's Laws to find Inverse Expression

- The complement or inverse of any Boolean expression can be found using DeMorgan's Laws.
- DeMorgan's Laws for n -variable expressions:

$$(X_1 + X_2 + X_3 + \cdots + X_n)' = X_1' X_2' X_3' \cdots X_n' \quad (2-25)$$

$$(X_1 X_2 X_3 \cdots X_n)' = X_1' + X_2' + X_3' + \cdots + X_n' \quad (2-26)$$

For example, for $n = 3$,

$$(X_1 + X_2 + X_3)' = (X_1 + X_2)' X_3' = X_1' X_2' X_3'$$

- The complement of the product is the sum of the complements.
- The complement of the sum is the product of the complements.

Complementing Boolean Expressions

Examples: Complementing Boolean expressions

Example 1

To find the complement of $(A' + B)C'$, first apply (2-13) and then (2-12).

$$[(A' + B)C']' = (A' + B)' + (C')' = AB' + C$$


Example 2

$$\begin{aligned} [(AB' + C)D' + E]' &= [(AB' + C)D']'E' && \text{(by (2-12))} \\ &= [(AB' + C)' + D]E' && \text{(by (2-13))} \\ &= [(AB')'C' + D]E' && \text{(by (2-12))} \\ &= [(A' + B)C' + D]E' && \text{(by (2-13)) (2-27)} \end{aligned}$$

Note that in the final expressions, the complement operation is applied only to single variables.

Complementing Boolean Expressions

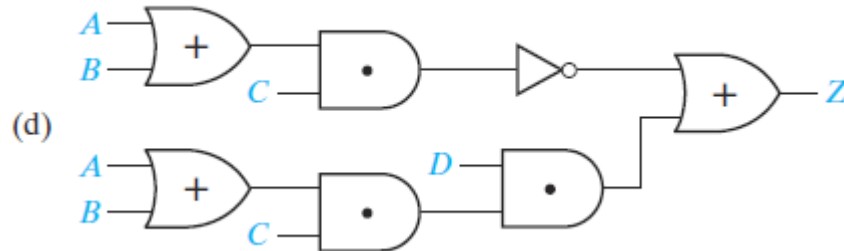Example 3: Find the output and design a simpler circuit that has the same output.



$$Z = [(A+B)C]' + (A+B)CD = [(A+B)C]' + D = A'B' + C' + D$$

(using elimination theorem $X + X'Y = X + Y$)